

# **ECE 3337 – Electronic Circuits**

Differential Amplifiers Lab Report

*Arnav Goyal - 251244778*

## Objectives

The objectives of this lab are:

1. To understand how to amplify weak (small) signals in the presence of noise.
2. To understand how a differential amplifier rejects noise and common mode signals.
3. To evaluate the roles of the components of a differential amplifier.
4. To test the operation of a current source in place of an emitter resistor.
5. To simulate the dc conditions of various differential amplifier circuits using MicroCap software.

## Prelab Information

*Calculations (unitless quantities are either mA, kOhm)*

Rearranging equation 3.2 to solve for  $I_{E1}$ :

$$I_{E1} = I_{E2} = \frac{I_{EE}}{2} = \frac{4}{2} = 2$$

Rearranging equation 3.4 to solve for  $R_E$ :

$$R_E = \frac{V_{B3} - V_{BE3} - V_{EE}}{I_{EE}} = \frac{-5 - 0.7 - (-10)}{4} = 1.075$$

Rearranging equation 3.3 to solve for  $R_{C1}$ :

$$R_{C1} = \frac{V_{CC} - V_{CE1} - V_{CE3} - I_{EE}R_E - V_{EE}}{I_{C1}} = \frac{10 - 4.5 - 4.5 - (4)(1.075) - (-10)}{2} = 3.35 = R_{C2}$$

Closest Std. Resistor Values are 1.1k, and 3.3k.

Small Signal Parameters

$$g_m = g_{m1} = g_{m2} = \frac{I_{C1}}{v_T} = \frac{2}{25} = 80, r_e = r_{e1} = r_{e2} = \frac{v_T}{I_{E1}} = \frac{25}{2} = 12.5$$

When input of Q2 is grounded:

$$i_e = \frac{v_{id}}{2r_e + \frac{2R_b}{\beta+1}} = \frac{v_{id}}{2(12.5) + \frac{2(10000)}{176}} = \frac{v_{id}}{138.6364} \Rightarrow v_{id} = 138.6364i_e$$

$$v_{o1} = -\alpha i_e R_{C1} = -\frac{175}{176} i_e (3.3) = -3.2813i_e$$

$$v_{o2} = 0$$

$$\frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = \frac{0 - (-3.2813i_e)}{138.6364i_e} = \frac{3.2813i_e}{138.6364i_e} = 23.668 = 27.483 \text{ dB}$$

Case where input of Q1 is grounded

$$i_e = \frac{v_{id}}{2r_e + \frac{2R_b}{\beta+1}} = \frac{v_{id}}{2(12.5) + \frac{2(10000)}{176}} = \frac{v_{id}}{138.6364} \Rightarrow v_{id} = 138.6364i_e$$

$$v_{o1} = 0$$

$$v_{o2} = \alpha i_e R_{C2} = \frac{175}{176} i_e (3.3) = 3.2813i_e$$

$$\frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = \frac{3.2813i_e - 0}{138.6364i_e} = \frac{3.2813i_e}{138.6364i_e} = 23.668 = 27.483 \text{ dB}$$


Input Impedance when Q2 is grounded

When Q2 is grounded, current still flows through the base resistances. So we include these and the emitter resistance of Q1 and Q2 in the calculations here.


$$R_{in} = 2(\beta + 1)r_e + 2R_b = 2(176)(12.5) + 2(10) = 24.4$$

## Plots
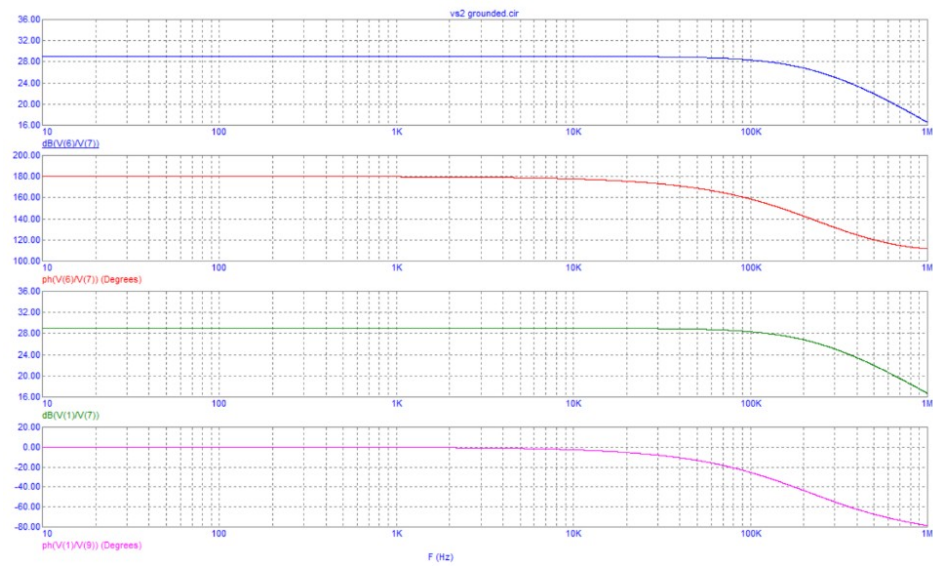
### Frequency Response of a Diff. Amplifier.


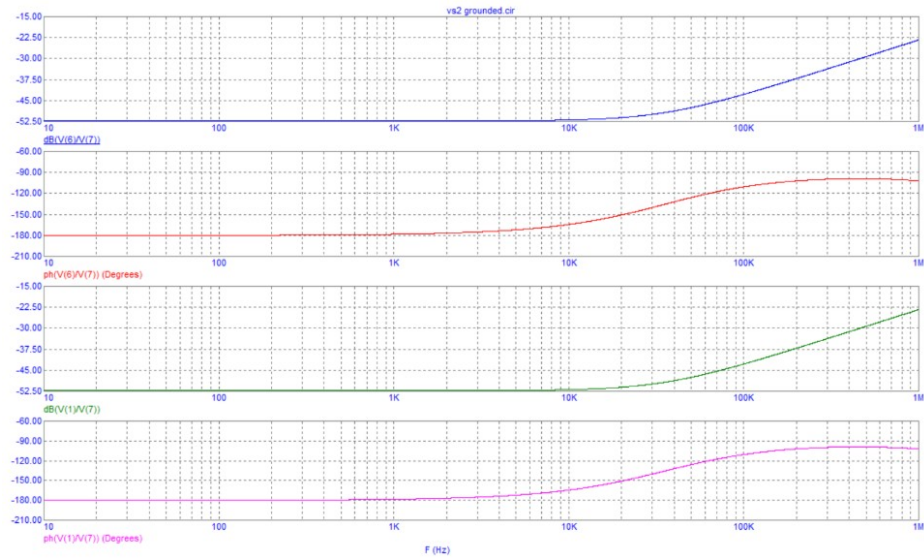
### Frequency Response of a Common Mode Diff. Amplifier



## Procedure & Results

1. Connect the differential amplifier shown in Figure 3.3 using calculated values of  $R_{C1} = R_{C2}$  and  $R_e$ . You will obtain better results if you 'match' the two transistors in the differential pair using the curve tracer output characteristics.
2. Use a dual voltage Power Supply and connect its POS terminal as  $V_{cc}$ , NEG terminal as  $V_{ee}$  and COM terminal as a common ground. Set the power supply voltage to 10V DC. Measure the DC quiescent point values. Use **Table 1** to compare the voltages and currents from your calculations and from the simulation with the experimental data. If your results are significantly different (more than 15%) from your calculated and simulated values, try to switch positions of the Q2 and Q3 BJTs and find out if the actual DC biasing provides closer to simulated results.

	Q1			Q2			Q3		
	$V_{CE}$ [V]	$V_{BE}$ [V]	$I_C$ [mA]	$V_{CE}$ [V]	$V_{BE}$ [V]	$I_C$ [mA]	$V_{CE}$ [V]	$V_{BE}$ [V]	$I_C$ [mA]
Calculation	4.5	0.7	2.0	4.5	0.7	2.0	4.5	0.7	4.0
Simulation	4.733	0.6863	1.851	4.733	0.6863	1.851	5.02	0.7091	3.732
Experiment	5.127	0.672	1.722	4.886	0.6965	1.784	4.988	0.686	3.652

Table 1: Differential Amplifier Biasing Conditions

3. Connect the signal generator (FG) to the Q1 input with the Q2 input connected to ground as it is shown in Figure 3.3. Increase the input signal to one input (Q1). Determine the maximum output signal the circuit will produce without distortion. Use a frequency of 1 kHz. Compare this result with the VCE of the two transistors in the differential pair and with VCC.
4. Set the frequency at 1 kHz and determine the input resistance as seen at Q1 with the input of Q2 connected to common ground.

5. With the input signal connected to one input and the second input grounded, determine the frequency response of the voltage gain (magnitude in dB and phase) to the collectors of Q1 and Q2. Set the amplitude of the Function Generator (FG) to 50mV. Sweep a frequency range from 50 Hz to 1 MHz and collect all data in **Table 2**.

$f$ [Hz]	$V_{in}$ [V]	$V_{O1}$ [V]	$\Theta_1$ [deg]	$A_{Q1}$ [dB]	$V_{O2}$ [V]	$\Theta_2$ [deg]	$A_{Q2}$ [dB]
50	0.056	1.42	179.6	28.082	1.42	-0.392	28.082
100	0.056	1.42	179.6	28.082	1.42	-0.394	28.082
200	0.056	1.42	176.7	28.082	1.42	-3.302	28.082
500	0.055	1.42	174.6	28.239	1.42	-5.403	28.239
800	0.055	1.44	174.2	28.360	1.42	-5.803	28.239
1k	0.055	1.44	173.5	28.360	1.42	-6.496	28.239
10k	0.054	1.40	172.0	28.275	1.40	-8.007	28.275
50k	0.054	1.22	141.4	27.079	1.22	-38.796	27.079
100k	0.054	0.90	123.7	24.437	0.90	-46.310	24.437
200k	0.054	0.54	99.67	20.000	0.53	-80.332	19.838
500k	0.053	0.23	81.56	0.23	0.22	-98.438	12.363
800k	0.053	0.14	67.52	0.14	0.14	-112.479	8.437
1M	0.053	0.11		0.11	0.106		6.021

Table 2: Experimental Frequency Response of a Differential Amplifier

- Connect both Ch1 of the oscilloscope and the Phase meter in parallel to the input signal. Connect both Ch2 of the oscilloscope and the Phase meter in parallel to the output 1 (Q1) signal. Read both instruments and then switch the "out" measurement terminal to the output 2 (Q2) signal. Change the frequency of the signal generator and repeat the measurements for both outputs. Note which output provides the inverting output and which one the non-inverting output
- Calculate the voltage gain  $A_{Q1}$ [dB] and  $A_{Q2}$ [dB] for both outputs of the differential amplifier, using Equation (3.5).
- Plot obtained voltage gain and phase data on top of your simulated Bode plots and compare the results
- Set the frequency at 1 kHz and interchange the two input connections. Determine the voltage gain to the collectors of Q1 and Q2.
- Connect both inputs to the same voltage source as it is shown in Figure 3.4 and make the necessary measurements to plot the frequency response of the common mode signal. Increase the input signal up to 6-7 V to be able to measure the output voltage. Vary the frequency from


50 Hz to 1 MHz and fill all data in **Table 3**. These results will give you an indication how well the differential amplifier rejects the common signal.

$f$ [Hz]	$V_{in}$ [V]	$V_{O1}$ [V]	$\Theta_1$ [deg]	$A_{Q1}$ [dB]	$V_{O2}$ [V]	$\Theta_2$ [deg]	$A_{Q2}$ [dB]
50	6.24	0.00	0.00	$-\infty$	0.00	0.00	$-\infty$
100	6.24	0.00	0.00	$-\infty$	0.00	0.00	$-\infty$
200	6.24	0.00	0.00	$-\infty$	0.00	0.00	$-\infty$
500	6.24	0.00	0.00	$-\infty$	0.00	0.00	$-\infty$
800	6.24	0.00	0.00	$-\infty$	0.00	0.00	$-\infty$
1k	6.32	0.04	0.00	-43.973	0.03	0.00	-46.472
10k	6.32	0.04	0.00	-43.973	0.04	0.00	-43.973
50k	6.32	0.04	0.00	-42.035	0.05	0.00	-42.035
100k	6.32	0.05	0.00	-36.929	0.08	0.00	-37.953
200k	6.32	0.09	0.00	-29.994	0.11	0.00	-35.186
500k	6.32	0.20	-115.7	-27.387	0.20	-129.3	-29.994
800k	6.32	0.27	-138.2	-26.187	0.28	-152.7	-27.071
1M	6.32	0.31	-149.5	-26.187	0.31	-163.2	-26.187

Table 3: Experimental Frequency Response of a Differential Amplifier in Common Mode

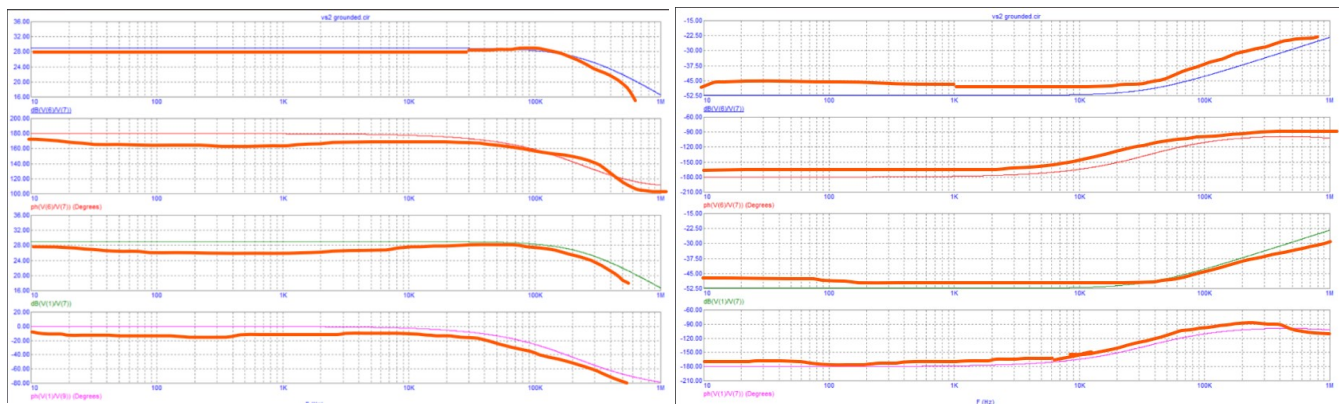11. Plot obtained voltage gain and phase data on top of your simulated Bode plots and compare the results.

Overall the results aligned very closely with simulation, the drawn lines are orange and are overlayed on top of the prelab plots. The plots are for regular (left) and common mode (right)



## Discussion

From this lab we learned about implementations of a Differential Amplifier in regular and in common-mode. Essentially a differential amplifier is a functional building block in analog design which serves to amplify a differential pair of signals or the difference between them. This basic block is very widely used in industry due to the noise immunity that a differential pair provides. Any EMI received by one trace, will be received by the other, allowing this EMI to cancel out at the convergence point where we only consider the difference between these two traces.

## Conclusion

In this lab, the DC Biasing values agreed with the simulated values. The amplifiers also acted in line with the expected theory of each configuration. Leading to good a good set of results discussed in the prior sections.